



Universidade Federal de Santa Catarina
Centro Tecnológico – CTC
Departamento de Engenharia Elétrica



“EEL5105 - Circuitos e Técnicas Digitais”

Prof. Héctor Pettenghi Roldán*

Hector@eel.ufsc.br

Florianópolis, março de 2016.

***Baseados nos slides do Professor Eduardo Bezerra e Eduardo Batista EEL5105 2015.2**

Estudo de caso: uso de processo explícito para implementar registrador com reset assíncrono, clock e sinal de enable

Deslocamento de vetor de entrada 1 bit à esquerda (1/2)

- sr_in recebe palavra de N bits (vetor de N bits). A cada
- pulso de clock, a palavra em sr_in é deslocada 1 bit para a
- esquerda, e copiada para sr_out, também de N bits.

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity desloc_1_bit_esq is
```

```
    generic ( N : natural := 64 );
```

```
    port      ( clk          : in std_logic;
```

```
               enable       : in std_logic;
```

```
               reset        : in std_logic;
```

```
               sr_in        : in std_logic_vector((N - 1) downto 0);
```

```
               sr_out       : out std_logic_vector((N - 1) downto 0)
```

```
    );
```

```
end entity;
```

Deslocamento de vetor de entrada 1 bit à esquerda (2/2)

architecture rtl of desloc_1_bit_esq is

signal sr: std_logic_vector ((N - 1) downto 0); -- Registrador de N bits
begin

process (clk, reset)
begin

if (reset = '0') then -- Reset assíncrono do registrador

sr <= (others => '0');

elsif (rising_edge(clk)) then -- Sinal de clock do registrador (subida)

if (enable = '1') then -- Sinal de enable do registrador

-- Desloca 1 bit para a esquerda. Bit mais significativo é perdido.

sr((N - 1) downto 1) <= sr_in((N - 2) downto 0);

sr(0) <= '0';


end if;

end if;

end process;


sr_out <= sr;

end rtl;

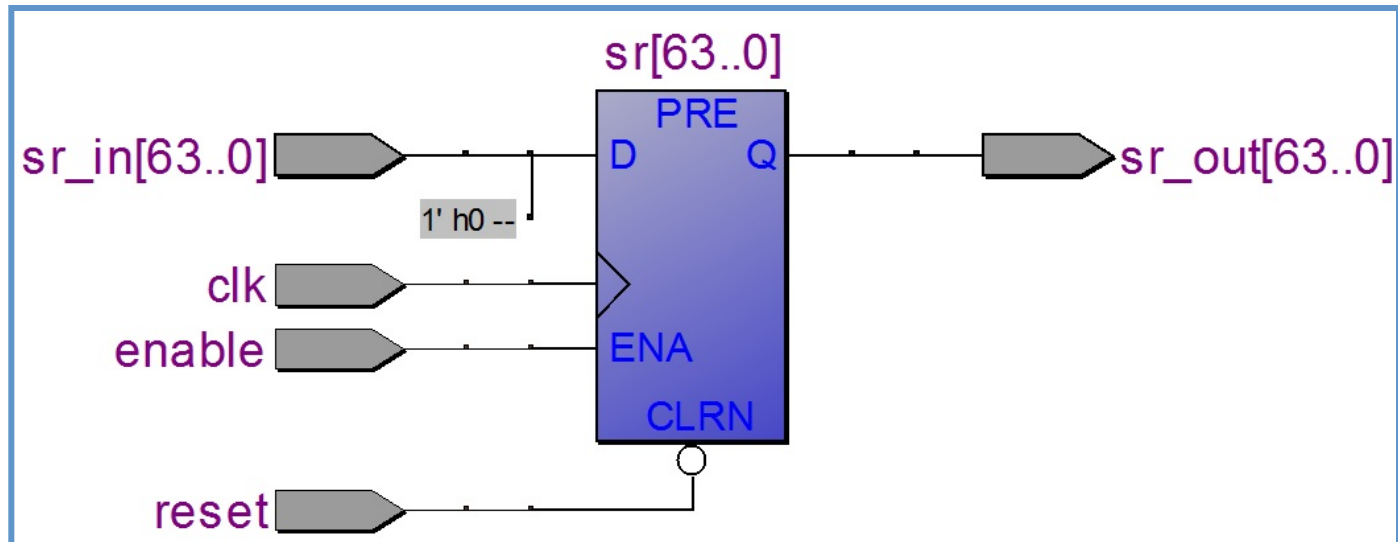

Deslocamento de vetor de entrada 1 bit à esquerda

Valor de entrada em *sr_in* = 93H

 

Valor de saída em *sr_out* = 26H


***Tarefa a ser realizada:
mini-calculadora com multiplicação e divisão por 2***

Tarefa – Descrição Textual


- Alterar a mini-calculadora desenvolvida nas aulas anteriores, de forma a realizar a “multiplicação por 2” e a “divisão por 2”.
- Utilizando um **registrador de deslocamento**, projetar um circuito para realizar operações de **divisão por 2** (*shift right*).
- Utilizando um **registrador de deslocamento**, projetar um circuito para realizar operações de **multiplicação por 2** (*shift left*).
- Substituir o componente que realiza a função **$F = \text{not } A$** pelo novo componente que realiza a multiplicação por 2.
- Substituir o componente que realiza a função **$F = A \text{ xor } B$** pelo novo componente que realiza a divisão por 2.

Atenção!! Nesse novo circuito existem dois componentes que utilizam apenas um operando, e dois componentes que utilizam dois operandos. **É preciso alterar a FSM para se adequar a essa situação!!**

Operandos
SW(7 downto 0)



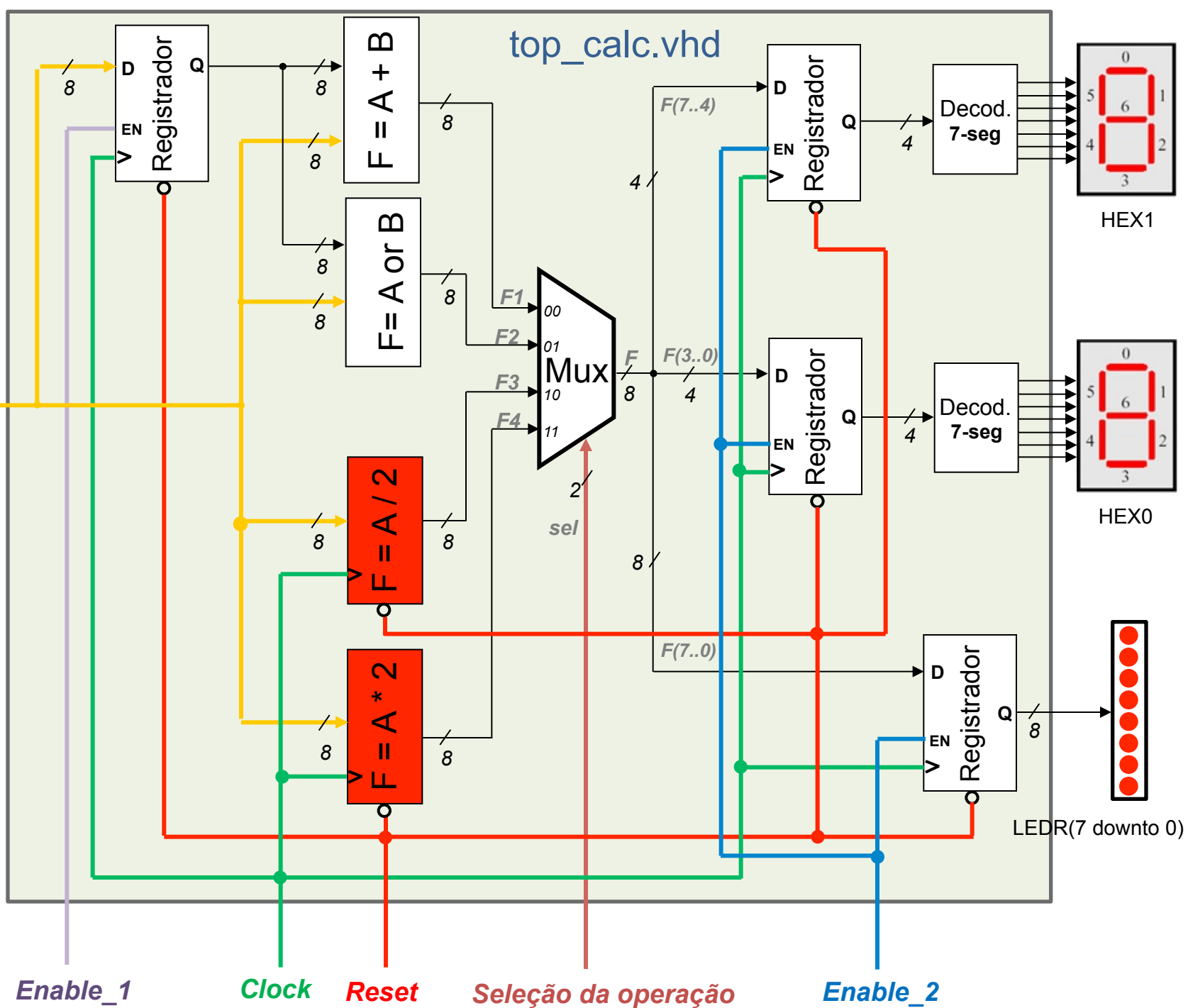


TOPO

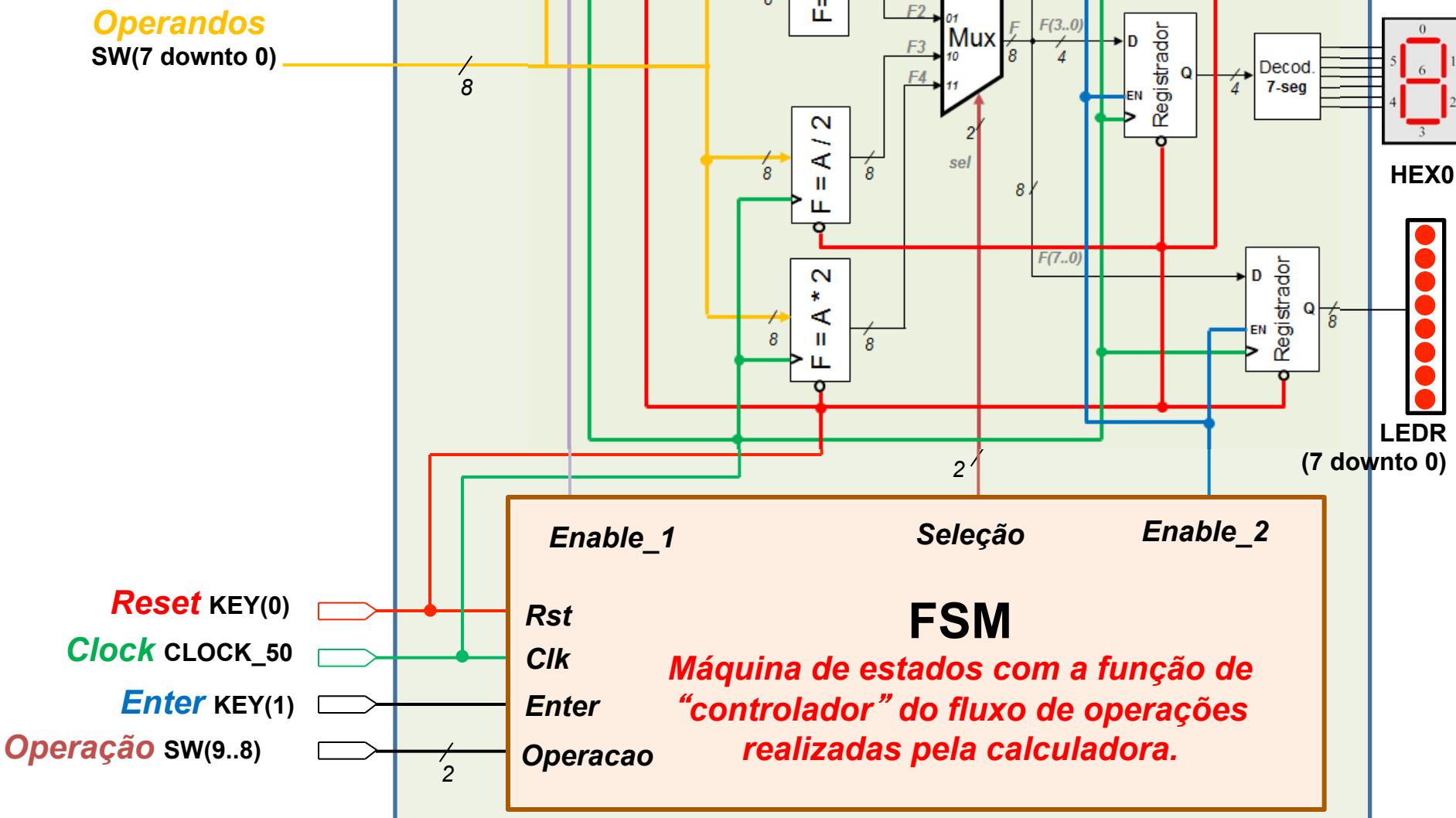

Outros templates de descrições em Quartus II

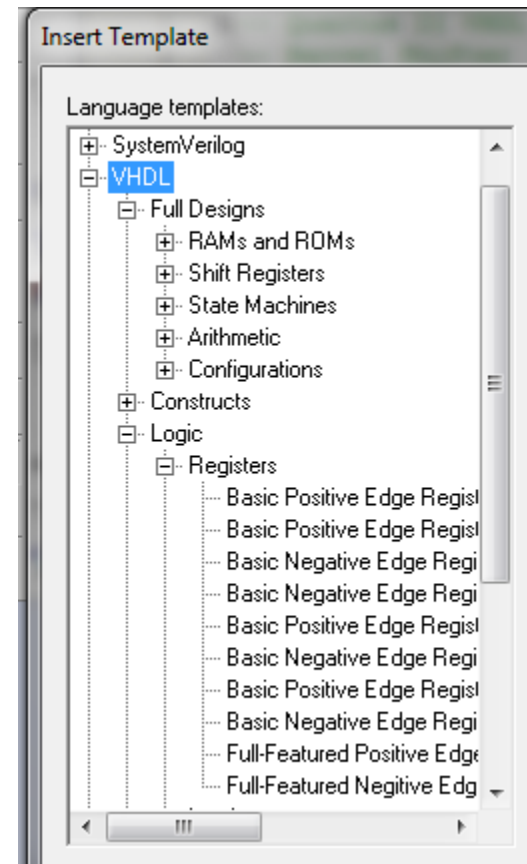 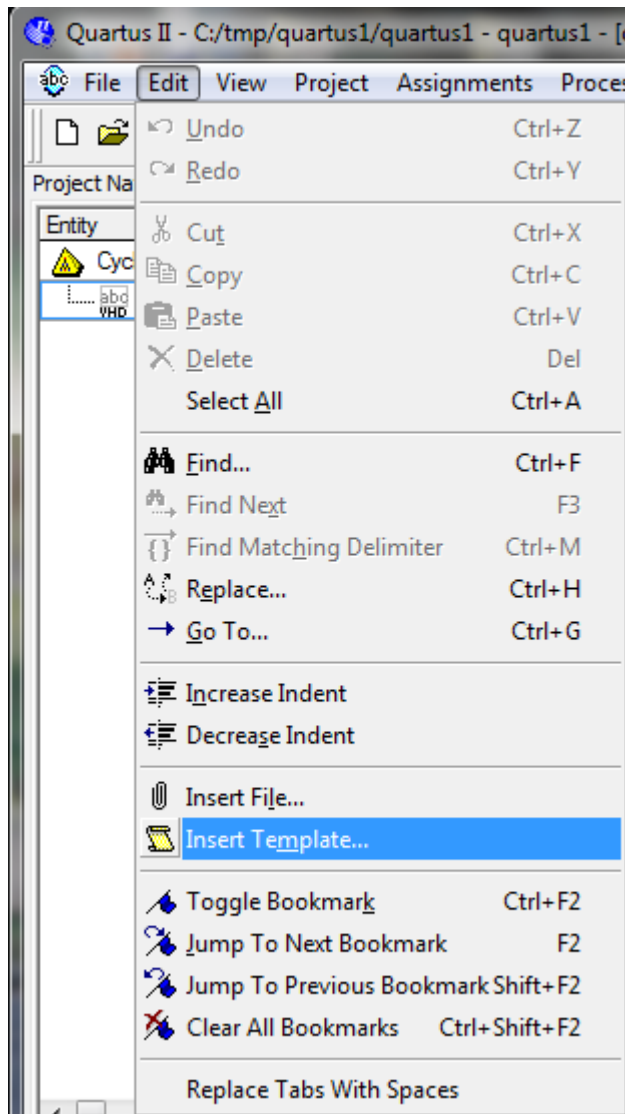Quartus II – Templates de descrições VHDL com processos




Basic Positive Edge Register with Asynchronous Reset and Clock Enable

```
process (<clock_signal>, <reset>)
begin
    -- Reset whenever the reset signal goes low, regardless
    -- of the clock or the clock enable
    if (<reset> = '0') then
        <register_variable> <= '0';
    -- If not resetting, and the clock signal is enabled,
    -- update the register output on the clock's rising edge
    elsif (rising_edge(<clock_signal>)) then
        if (<clock_enable> = '1') then
            <register_variable> <= <data>;
        end if;
    end if;
end process;
```

Basic Positive Edge Register with Asynchronous Reset
 
```
process (CLK, RST)
begin
    -- Reset whenever the reset signal goes low, regardless
    -- of the clock
    if (RST = '0') then
        Q <= '0';
    -- If not resetting update the register output
    -- on the clock's rising edge
    elsif (CLK'event and CLK = '1') then
        Q <= D;
    end if;
end process;
```



Binary counter (1/2)

-- Binary counter

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

entity binary_counter is

 generic (MIN_COUNT : natural := 0;
 MAX_COUNT : natural := 255);

 port (

 clk : in std_logic;

 reset : in std_logic;

 enable : in std_logic;

 q: out integer range MIN_COUNT to MAX_COUNT
);

end entity;

Binary counter (2/2)

```
architecture rtl of binary_cunter is
begin
    process (clk)
        variable cnt: integer range MIN_COUNT to MAX_COUNT;
    begin
        if (rising_edge(clk)) then
            if (reset = '1') then
                -- Reset counter to 0
                cnt := 0;
            elsif enable = '1' then
                cnt := cnt + 1;
            end if;
        end if;
        -- Output the current count
        q <= cnt;
    end process;
end rtl;
```

Basic Shift Register with Asynchronous Reset (1/2)

-- One-bit wide, N-bit long shift register with asynchronous reset

library ieee;

use ieee.std_logic_1164.all;

entity basic_shift_register_asynchronous_reset is

generic (NUM_STAGES : natural := 256);

port (clk : in std_logic;
enable : in std_logic;
reset : in std_logic;
sr_in : in std_logic;
sr_out : out std_logic
);

end entity;

Basic Shift Register with Asynchronous Reset (2/2)

```
architecture rtl of basic_shift_register_asynchronous_reset is
    type sr_length is array ((NUM_STAGES-1) downto 0) of std_logic;
    signal sr: sr_length;           -- Declare the shift register
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            sr <= (others => '0');
        elsif (rising_edge(clk)) then
            if (enable = '1') then
                -- Shift data by one stage; data from last stage is lost
                sr((NUM_STAGES-1) downto 1) <= sr((NUM_STAGES-2) downto 0);
                sr(0) <= sr_in;
            end if;
        end if;
    end process;
    sr_out <= sr(NUM_STAGES-1);
end rtl;
```

Four-State Mealy State Machine (1/5)

- A Mealy machine has outputs that depend on both the state and the
- inputs. When the inputs change, the outputs are updated immediately,
- without waiting for a clock edge. The outputs can be written more than
- once per state or per clock cycle.

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity four_state_mealy_state_machine is
```

```
port (
```

```
    clk      : in std_logic;
```

```
    input    : in std_logic;
```

```
    reset    : in std_logic;
```

```
    output   : out std_logic_vector (1 downto 0)  
);
```

```
end entity;
```

Four-State Mealy State Machine (2/5)

```
architecture rtl of four_state_mealy_state_machine is
    -- Build an enumerated type for the state machine
    type state_type is (s0, s1, s2, s3);
    signal state : state_type;      -- Register to hold the current state
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            state <= s0;
        elsif (rising_edge(clk)) then
            -- Determine the next state synchronously, based on
            -- the current state and the input
            case state is
                when s0 =>
                    if input = '1' then state <= s1;
                    else state <= s0;
                    end if;
            end case;
        end if;
    end process;
end;
```

Four-State Mealy State Machine (3/5)

```
when s1 =>
    if input = '1' then    state <= s2;
    else                  state <= s1;
    end if;
when s2 =>
    if input = '1' then    state <= s3;
    else                  state <= s2;
    end if;
when s3 =>
    if input = '1' then    state <= s3;
    else                  state <= s1;
    end if;
end case;
end if;
end process;
```

Four-State Mealy State Machine (4/5)

- Determine the output based only on the current state
- and the input (do not wait for a clock edge).

```
process (state, input)
begin
    case state is
        when s0 =>
            if input = '1' then
                output <= "00";
            else
                output <= "01";
            end if;
```

Four-State Mealy State Machine (5/5)

```
when s1 =>
    if input = '1' then    output <= "01";
    else                  output <= "11";
    end if;
when s2 =>
    if input = '1' then    output <= "10";
    else                  output <= "10";
    end if;
when s3 =>
    if input = '1' then    output <= "11";
    else                  output <= "10";
    end if;
end case;
end process;
end rtl;
```

Four-State Moore State Machine (1/4)

- A Moore machine's outputs are dependent only on the current state.
- The output is written only when the state changes. (State transitions are synchronous.)

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity four_state_moore_state_machine is  
  port (
```

```
    clk      : in std_logic;
```

```
    input    : in std_logic;
```

```
    reset    : in std_logic;
```

```
    output   : out std_logic_vector (1 downto 0)  
  );
```

```
end entity;
```

Four-State Moore State Machine (2/4)

```
architecture rtl of four_state_moore_state_machine is
    -- Build an enumerated type for the state machine
    type state_type is (s0, s1, s2, s3);
    signal state : state_type;      -- Register to hold the current state
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            state <= s0;
        elsif (rising_edge(clk)) then
            -- Determine the next state synchronously, based on
            -- the current state and the input
            case state is
                when s0 =>
                    if input = '1' then state <= s1;
                    else state <= s0;
                    end if;
            end case;
        end if;
    end process;
end;
```


Four-State Moore State Machine (3/4)

```
when s1 =>
    if input = '1' then state <= s2;
    else                 state <= s1;
    end if;
when s2 =>
    if input = '1' then state <= s3;
    else                 state <= s2;
    end if;
when s3 =>
    if input = '1' then state <= s3;
    else                 state <= s1;
    end if;
end case;
end if;
end process;
```

Four-State Moore State Machine (4/4)

-- Output depends solely on the current state.

```
process (state, input)
begin
    case state is
        when s0 =>
            output <= "00";
        when s1 =>
            output <= "01";
        when s2 =>
            output <= "10";
        when s3 =>
            output <= "11";
    end case;
end process;
end rtl;
```

Single-port RAM with initial contents (1/4)

-- Single-port RAM with single read/write address and initial contents

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all ;

entity single_port_ram_with_init is

generic (DATA_WIDTH : natural := 8;

ADDR_WIDTH : natural := 6);

port (

clk : in std_logic;

addr: in natural range 0 to 2**ADDR_WIDTH - 1;

data: in std_logic_vector((DATA_WIDTH-1) downto 0);

we : in std_logic := '1';

q : out std_logic_vector((DATA_WIDTH -1) downto 0)
);

end single_port_ram_with_init;

Single-port RAM with initial contents (2/4)

architecture rtl **of** single_port_ram_with_init **is**

-- Build a 2-D array type for the RAM

subtype word_t is std_logic_vector((DATA_WIDTH-1) downto 0);

type memory_t is array(2**ADDR_WIDTH-1 downto 0) of word_t;

function init_ram **return** memory_t **is**

variable tmp : memory_t := (others => (others => '0'));

begin

for addr_pos **in** 0 **to** 2**ADDR_WIDTH - 1 **loop**

 -- Initialize each address with the address itself

 tmp(addr_pos) := std_logic_vector(to_unsigned(addr_pos,
 DATA_WIDTH));

end loop;

return tmp;

end init_ram;

Single-port RAM with initial contents (3/4)

- Declare the RAM signal and specify a default value.
- Quartus II will create a memory initialization file (.mif) based on
- the default value.

```
signal ram : memory_t := init_ram;
```

- Register to hold the address

```
signal addr_reg : natural range 0 to 2**ADDR_WIDTH-1;
```

Single-port RAM with initial contents (4/4)

```
begin
    process(clk)
    begin
        if (rising_edge(clk)) then
            if (we = '1') then
                ram(addr) <= data;
            end if;
            -- Register the address for reading
            addr_reg <= addr;
        end if;
    end process;
    q <= ram(addr_reg);
end rtl;
```